

JEWELRY MAKING INSTRUCTION

www.moddahobbykits.com

WARNING

- This kit contains small parts and sharp tools. Keep away from children
- Activity recommended for Adults and Teenagers 12+

Warnings for Cutting Tools

- Please keep out of children.
- Always keep points away from fingers and body. Handle with care. Use with adult supervision.
- Please do not use to cut hard material and steel wire, etc.
- Products have functional sharp points. Contact may result in injury.
- Please use safety items, such as safety glasses and protective gloves.

The Kit Contains

Pliers and Other Tools



Findings





Making Your First Single Drop Earrings

Materials

- 1 Flat nose pliers
- Beads

- 2 Headpins
- 2 Earwires



1- String your beads onto the head pin, starting with the bottom bead and ending at the top



2- Bend the wire at a 90 degree angle with your flat nose pliers



 Leave about 3/8" (1cm) tail



4- Cut the head pin with your flat nose pliers



5- Grasp the end of the wire with your flat nose pliers



6- Rotate your pliers slightly by turning your wrist clockwise, until it forms a complete loop



7- Open up the loop with your flat nose pliers, gently twisting the loop up



8- Take the earwire and thread the loop of the earwire through the open loop



9- Close the open hook using your pliers. Make it nice and tight so the earrings won't fall apart. And your first earrings are ready!

Making Your First Bracelet With Elastic Cord

Materials

• 1 Flat Nose Pliers

Beads

• Elastic nylon cord



1- Select your beads and decide on a design before putting the beads on the elastic cord



2- Measure your elastic cord: Take the elastic cord and wrap it one and a half times around your wrist.Cut it with your pliers



3- Start threading your beads







4- Check the length of bracelet before making the knot. The first and last bead should be touching. If you see any cord or gaps, you will need more beads

5- Make a couple of surgeon's knots or a couple overhand knots in your elastic cord , being careful not to pull too tightly. Then slide the knot under the bead

6- Your bracelet is ready!

Making Your First Wire Wrapped Bracelet and Necklace

Materials

- 1 Flat nose pliers
- 2 Crimp beads
- Beads

- 1 Jump ring
- 1 Lobster clasp
- Beading wire



 First select your beads and arrange the pattern you want



2- Measure your beading wire around your wrist or neck, then add 4-5 inches

3- Cut the beading wire with your flat nose pliers



4- Thread one crimp bead and one lobster clasp



5- Slip the wire through the clasp loop and bring the end of the wire back through the crimp bead



6- Take your flat nose pliers, simply grasp the crimp bead and squeeze gently and pull to be sure it is secure



7- Now start threading your beads according to your pattern until you reach other end. Be sure leave about 3-4 inches of the wire at the end



8- To hide the end of the wire, thread it back through some of the beads. or cut the excess with your flat nose pliers



9- Tight all of your beads by pulling on the tail end of the loose wire and then check the fit of the necklace / bracelet. Add beads if necessary



10- Thread one crimp bead, then thread the jump ring



11- Slip the wire through the jump ring loop and bring the end of the wire back through the crimp bead



12- Hide the excess wire into the next beads





14- Use your flat nose pliers to trim off excess wire



15- That's it, your necklace/bracelet is ready

13- Take your flat nose pliers, simply grasp the crimp bead with the flat section of your pliers and squeeze gently and pull to be sure it is secure

Making Your First Memory Wire Bracelet

Materials

- 1 Flat Nose Pliers
- Memory Wire

Beads



1- Select your beads and arrange them on the table in a preferred pattern



2- Use your flat nose pliers to cut the length of memory wire one wrap or several , what you want for your bracelet



3- Hold the end of the wire, and use your flat nose pliers to create a small bend (this is the beginning of your end loop).



4- Form the end loop by taking your flat nose pliers and rotating it inwards



5- At the other end of the wire thread your beads, once you are almost at the end stop adding beads



6- Use the flat nose pliers to create another end loop to finish the bracelet. That's it! You've just created your own beaded memory wire bracelet





Scan For Review

Don't Forget to Add Photos of Your First Jewelry to Your Review on Amazon!