Don't Forget To Visit Our Website To Access Your

JEWELRY MAKING VIDEO COURSE!



www.moddahobbykits.com

WARNING

- This kit contains small parts and sharp tools.
 Keep away from children
- Activity recommended for Adults and Teenagers 12+

Warnings for Cutting Tools

- Please keep out of children.
- Always keep points away from fingers and body. Handle with care. Use with adult supervision.
- Please do not use to cut hard material and steel wire, etc.
- Products have functional sharp points. Contact may result in injury.
- Please use safety items, such as safety glasses and protective gloves.

The Kit Contains

3 Pliers and Cutters



Wire, Cord and Chain



300 Findings







50 Jump rings



And Lots of Lovely Beads and Charms...



Making Your First Single Drop Earrings

Materials

- 1 Round nose pliers
- 1 Chain nose pliers
- 1 Side cutters

- 2 Headpins
- 2 Earwires
- Beads



1- String your beads onto the head pin, starting with the bottom bead and ending at the top



2- Bend the wire at a 90 degree angle with your chain nose pliers



3- Leave about 3/8" (1cm) tail



4- Cut the head pin with your side-cutter



5- Grasp the end of the wire with your round nose pliers



6- Rotate your pliers slightly by turning your wrist clockwise, until it forms a complete loop



7- Open up the loop with your chain nose pliers, gently twisting the loop up



8- Take the earwire and thread the loop of the earwire through the open loop



9- Close the open hook using your pliers. Make it nice and tight so the earrings won't fall apart. And your first earrings are ready!

Making Your First Bracelet With Elastic Cord

Materials

- 1 Side Cutters
- Elastic nylon cord

Beads



1- Select your beads and decide on a design before putting the beads on the elastic cord



2- Measure your elastic cord: Take the elastic cord and wrap it one and a half times around your wrist.Cut it with your side cutters



3- Start threading your beads



4- Check the length of bracelet before making the knot. The first and last bead should be touching. If you see any cord or gaps, you will need more beads



5- Make a couple of surgeon's knots or a couple overhand knots in your elastic cord, being careful not to pull too tightly. Then slide the knot under the bead



6- Your bracelet is ready!

Making Your First Wire Wrapped Bracelet and Necklace

Materials

- 1 Round nose pliers
- 1 Chain nose pliers
- 1 Side cutters
- 2 Crimp beads

- 1 Jump ring
- 1 Lobster clasp
- · Beading wire
- Beads




1- First select your beads and arrange the pattern you want



2- Measure your beading wire around your wrist or neck, then add 4-5 inches



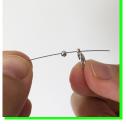3- Cut the beading wire with your side cutters



4- Thread one crimp bead and one lobster clasp



5- Slip the wire through the clasp loop and bring the end of the wire back through the crimp bead



6- Take your chain nose pliers, simply grasp the crimp bead and squeeze gently and pull to be sure it is secure




7- Now start threading your beads according to your pattern until you reach other end.
Be sure leave about 3-4 inches of the wire at the end



8- To hide the end of the wire, thread it back through some of the beads. or cut the excess with your side cutters



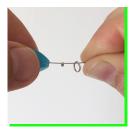9- Tight all of your beads by pulling on the tail end of the loose wire and then check the fit of the necklace / bracelet .Add beads if necessary



10- Thread one crimp bead, then thread the jump ring



11- Slip the wire through the jump ring loop and bring the end of the wire back through the crimp bead



12- Hide the excess wire into the next beads



13- Take your chain nose pliers, simply grasp the crimp bead with the flat section of your pliers and squeeze gently and pull to be sure it is secure



14- Use your cutter to trim off excess wire



15- That's it, your necklace/bracelet is ready

Making Your First Memory Wire Bracelet

Materials

- 1 Side cutters
- Memory Wire
- 1 Chain nose Pliers

- 1 Round Nose Pliers
- Beads



1- Select your beads and arrange them on the beading mat in a preferred pattern



2- Use your side cutters to cut the lenght of memory wire one wrap or several , what you want for your bracelet



3- Hold the end of the wire, and use your chain nose pliers to create a small bend (this is the beginning of your end loop).



4- Form the end loop by taking your round nose pliers and rotating it inwards



5- At the other end of the wire thread your beads, once you are almost at the end stop adding beads



6- Use the chain nose and round nose pliers to create another end loop to finish the bracelet. That's it! You've just created your own beaded memory wire bracelet





Don't Forget to Add
Photos of Your First
Jewelry to Your Review
on Amazon!